
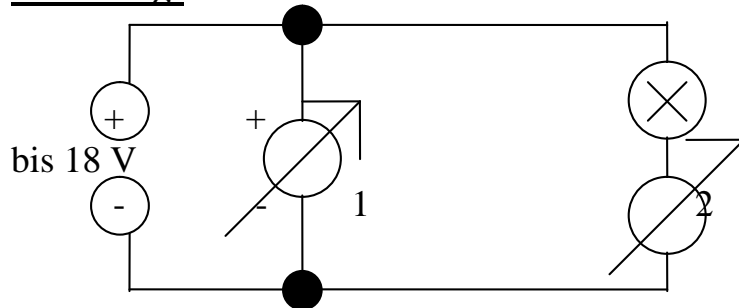


## Widerstand einer Glühlampe

### Schaltung:

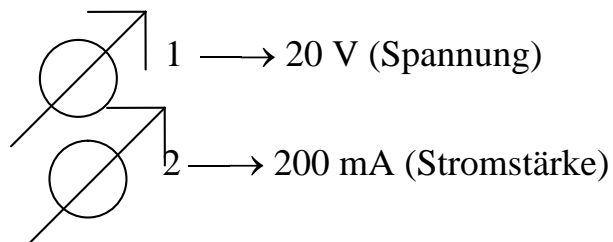

### Meßbereich:



### Messungen

U(V)	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
I (A)	10	20	29	34	39	43	48	50	54	57	61	64	67	70	71

